

Reviewing Key Terms

1. A(n) _____ cell consists of two _____ and a(n) _____.
2. The lithium ion cell in a camera is classified as a dry cell and a(n) _____.
3. If there is no current in a circuit that is attached to a source of electricity, it is a(n) _____.
4. The _____ is a unit that is equivalent to a coulomb per second.
5. Any device that transforms electrical energy into heat or other forms of energy is called a(n) _____.
6. In a(n) _____, the current divides _____ among different pathways.
7. The ratio of potential difference to current is called _____.
8. The difference between a wet cell and a dry cell is _____

9. The difference between a cell and a battery is _____

10. A fuel cell is different from other types of cells because _____

11. A secondary cell is a renewable source of energy because _____
_____.
12. Static electricity is an electric charge that _____

Current electricity is an electric charge that _____
13. Use the chart to determine which wire has a higher resistance.

	Wire 1	Wire 2	Which Has More Resistance?
Length of Wire	long	short	
Diameter	thin	thick	
Material	silver	copper	
Overall			

14. The current in a series connection travels _____, but the current in a parallel connection _____.

15. **Circle** ways you could increase the current in a circuit.

open some switches

add more loads in parallel

remove a cell or battery

add more loads in series

remove loads


add another cell or battery

16. State four properties of a wire that affect the resistance of the wire.


Determine if each change will increase or decrease the resistance of the wire.

Change	Increase or Decrease the Resistance?
Increase the length of the wire	
Increase the diameter of the wire	
Using a non-metal instead of a metal to make the wire	
Increase the temperature	

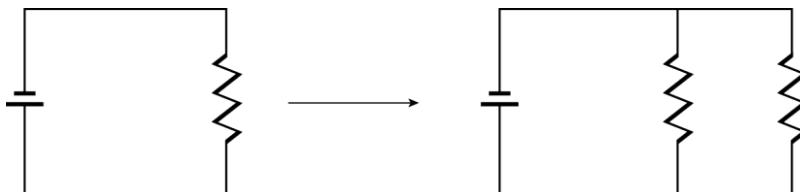
17. Does adding a resistor in parallel increase or decrease the total resistance in the circuit? Why?



18. Examine the graphs below.

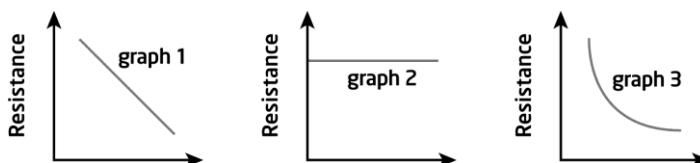

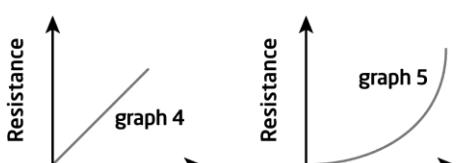a. If each horizontal axis represents the length of a wire, which graph is the relationship between resistance and length? Explain your answer.




b. If each horizontal axis represents the current, which graph represents a conductor that obeys Ohm's law? Explain your answer.

19. An experiment was done on a circuit in a flashlight. The data are recorded in the table below.

a. Plot the data. Put the potential difference on the vertical axis and the current on the horizontal axis. Give your graph a title.

Measurements in a Flashlight Circuit

Number of Cells	Potential Difference (V)	Current (A)
1	1.52	0.10
2	3.01	0.15
3	4.47	0.18
4	5.99	0.20

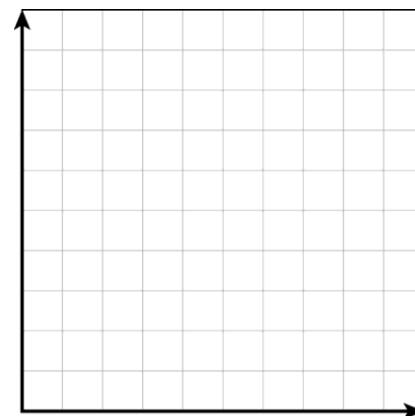


b. Draw the line of best fit for the data.

c. With one cell in the circuit, the bulb did not work. When there were four cells, the bulb glowed brightly. This is because _____.

d. The _____ of the graph is the resistance of the filament. The resistance _____ as the temperature of the filament _____.

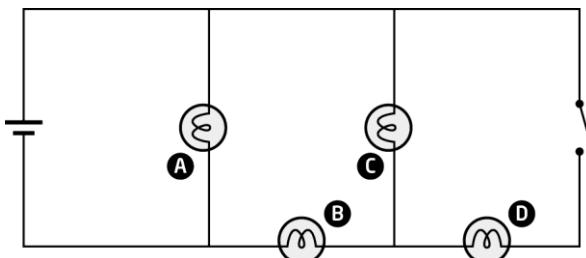20. Look at the circuit diagram below. Which bulb(s) will be off if the switch is in the open position? State your reasoning.



21. Two different flashlight bulbs (A and B) have filaments of the same material. The filament in bulb A is longer than the filament in bulb B. They are connected in a series to a 6 V battery. Use the correct sign (<, >, or =) to fill in the blanks.

a. brightness in bulb A _____ brightness in bulb B

b. current in bulb A _____ current in bulb B

c. potential difference between the terminals in bulb A _____ potential difference between the terminals in bulb B

d. resistance in bulb A _____ resistance in bulb B